

Contents

dc EXPERIMENTS

Math Review 1

- 1 Resistors and the Color Code 13
- 2 The dc Power Supply and dc Meters 21
- 3 Series dc Circuits 31
- 4 Parallel dc Circuits 39
- 5 Rheostats and Potentiometers 47
- 6 Series-Parallel dc Circuits 59
- 7 Methods of Analysis 67
- 8 Superposition Principle (dc) 75
- 9 Thevenin's Theorem and Maximum Power Transfer 85
- 10 Norton's Theorem and Source Conversions 97
- 11 Capacitors 105
- 12 R - L and R - L - C Circuits with a dc Source Voltage 117
- 13 Design of a dc Ammeter and Voltmeter and Meter Loading Effects 125
- 14 Wheatstone Bridge and Δ -Y Conversions 135
- 15 Ohmmeter Circuits 143

ac EXPERIMENTS

- Math Review 155
- 1** The Oscilloscope 167
- 2** *R-L-C* Components 181
- 3** Frequency Dependence of *R-L-C* Components 193
- 4** Frequency Response of *R-L* and *R-C* Networks 201
- 5** The Oscilloscope and Phase Measurements 213
- 6** Series Sinusoidal Circuits 229
- 7** Parallel Sinusoidal Circuits 243
- 8** Series-Parallel Sinusoidal Circuits 255
- 9** Thevenin's Theorem and Maximum Power Transfer 265
- 10** Series Resonant Circuits 273
- 11** Parallel Resonant Circuits 283
- 12** The Transformer 293
- 13** Pulse Waveforms 301
- 14** Currents and Voltages in Balanced Three-Phase Systems 313
- 15** Power Measurements in Three-Phase Systems 321

Parts List for the Experiments 331

APPENDICES

- I** Resistor Color Coding 335
- II** Capacitor Color Coding 337
- III** Resistance Measurements (VOM) 339
- IV** Proper Use of the VOM Multimeter 341
- V** Scientific Notation and Trigonometric Identities 343