



Contents

Preface	5
Used graphical symbols and abbreviations	7
Index.....	8
DC networks.....	9
1. Equivalent resistance, Ohm's and Kirchhoff's laws in DC networks.....	11
2. Mesh and Node Analyses in DC networks.....	35
AC networks.....	51
3. One-phase networks.....	53
4. Mesh and Node Analyses in 1-phase networks.....	67
5. Two-port networks.....	79
References.....	99