

# Contents

PREFACE

vii

INTRODUCTION

ix

## PART I: EXERCISES

### (A) Lumped Element Circuits

#### CHAPTER

Notation	3
1 Passive circuits	5
2 Amplifiers at high and audio frequencies	28
3 Feedback and stability	69
4 Non-linear circuits and switching	81
5 Noise	99

### (B) Transmission Lines and High Frequencies

Notation	111
6 Transmission lines	113
7 Power matching	133
8 Use of the Smith chart	147
9 Free and guided waves	167
10 The resonant cavity	188

## PART II: PROBLEMS

#### PROBLEM

1 Push-pull and distortion	205
2 Transistor differential amplifier	214
3 Differential amplifier	223
4 Two-stage transistor amplifier	231
5 L.T. transistor supply	239
6 H.F. amplifier	246
7 Delay line oscillator	261
8 Q-meter for magnetic resonance	266
9 Q-multiplier circuit	272
10 The gyrator	284
11 Phase sensitive detector	296
12 The diode circuit	302
13 Improvement of signal to noise ratio	311
14 Matching of a transmission line to a generator	321
15 Matching with two stubs	326

16	Matching band-width	333
17	Resonant load on a line	340
18	Matching in a wave guide	348
19	Matching with quarter-wave steps	352
20	Resonant systems	359
21	<i>Q</i> -factor of a rectangular cavity	375
22	Measurement of dielectric constant	383
23	Resonant cavity	391
24	Cavity equivalent circuits	400
25	Investigation of the resonant cavity	410
26	Cavities coupled by a length of line	414
	<b>INDEX</b>	427
	<b>OTHER TITLES IN THE SERIES IN NATURAL PHILOSOPHY</b>	429