

Contents

<i>Preface</i>	vii
1. Introduction	1
1.1 What are Digital Systems	1
1.2 How are Digital Systems Realised?	2
1.3 Binary Representation of Quantities	3
1.4 Serial and Parallel Data	4
1.5 Comparison of Analogue and Digital Systems	4
2. Review of Combinational-logic Techniques	5
2.1 Logic Levels	5
2.2 Gates	6
2.3 The Karnaugh Map	12
2.4 Partitioning	20
2.5 Iterative Circuits	22
2.6 Multiple Outputs	23
2.7 Concluding Remarks	24
2.8 Examples	24
References	28
3. Introduction to Sequential Systems	29
3.1 Fundamental Concepts	29
3.2 Storage Devices	32
3.3 Sequential Sub-systems	38
3.4 Intuitive Design of Sequential Systems	47
3.5 Examples	49
References	53
4. Asynchronous Sequential Systems	54
4.1 Basic Concepts	54
4.2 Analysis Techniques	57
4.3 Races and Hazards	63
4.4 System Design	68
4.5 Examples	87
References	102

5. Synchronous Sequential Systems	104
5.1 Advantages and Disadvantages of Synchronous Systems	104
5.2 Preliminary Design	106
5.3 Flow-chart Method of Design	109
5.4 Pictorial Aids	119
5.5 State Assignment	124
5.6 Examples	126
References	131
6. Practical Design Considerations	132
6.1 Initial Specification	132
6.2 Detailed Design	132
6.3 Prototype Development	134
6.4 Printed-circuit Boards	134
6.5 Testing and Documentation	136
6.6 Conclusion	136
References	137
<i>Appendix</i>	139
<i>Index</i>	141