

# Contents

## 1 General Background

|                                     |   |
|-------------------------------------|---|
| 1.1 Need                            | 1 |
| 1.2 Single Balance Stage            | 3 |
| 1.3 Common Signal Rejection         | 3 |
| 1.4 Differential Amplifier          | 5 |
| 1.5 Differential and Common Signals | 5 |
| 1.6 Historical Notes                | 7 |

## 2 Terminal Quantities

|                                    |    |
|------------------------------------|----|
| 2.1 Comments                       | 9  |
| 2.2 Configuration                  | 9  |
| 2.3 Linear Analysis                | 10 |
| 2.4 Linear Operation               | 12 |
| 2.5 New Port Variables             | 12 |
| 2.6 Amplifier Operation            | 15 |
| 2.7 Signal Source                  | 15 |
| 2.8 Signal Load                    | 21 |
| 2.9 Signal Source-Load Combination | 25 |

## 3 Single-Stage Static Design

|                                                   |    |
|---------------------------------------------------|----|
| 3.1 Introduction                                  | 28 |
| 3.2 Circuit Bisection                             | 29 |
| 3.3 Graphical Design                              | 30 |
| 3.4 Design Example                                | 33 |
| 3.5 Field-Effect Transistors (FET) Circuit Design | 35 |
| 3.6 Electron Tube Circuit Design                  | 37 |
| 3.7 Source Bias Arrangements                      | 39 |
| 3.8 Temperature Effects                           | 39 |

## **x Contents**

### **4 Small-Signal Operation**

|                                    |    |
|------------------------------------|----|
| 4.1 Comments                       | 50 |
| 4.2 General Differential Operation | 50 |
| 4.3 General Common Operation       | 55 |
| 4.4 Discrimination Ratios          | 57 |
| 4.5 Source Dissymmetry             | 57 |
| 4.6 Load Dissymmetry               | 58 |
| 4.7 General Dissymmetry            | 60 |
| 4.8 Recapitulation                 | 64 |

### **5 Circuit Modifications**

|                                     |    |
|-------------------------------------|----|
| 5.1 Comments                        | 66 |
| 5.2 Constant-Current Source         | 66 |
| 5.3 Constant-Current Design Example | 69 |
| 5.4 Feedback Current Source         | 70 |
| 5.5 Darlington Input                | 72 |
| 5.6 Balance Circuits                | 80 |

### **6 Small-Signal Performance**

|                                                              |    |
|--------------------------------------------------------------|----|
| 6.1 Comments                                                 | 81 |
| 6.2 Equivalent Circuits                                      | 81 |
| 6.3 Bipolar Transistor Differential Amplifier Operation      | 84 |
| 6.4 Bipolar Transistor with Constant-Current Source          | 88 |
| 6.5 Field-Effect Transistor Differential Amplifier Operation | 91 |
| 6.6 Unsymmetrical Bipolar Transistor Differential Amplifier  | 97 |

### **7 Large-Signal Operation**

|                      |     |
|----------------------|-----|
| 7.1 Comments         | 111 |
| 7.2 Without Feedback | 111 |
| 7.3 With Feedback    | 115 |
| 7.4 Power Output     | 119 |

### **8 Multistage Amplifiers**

|                                |     |
|--------------------------------|-----|
| 8.1 Introduction               | 126 |
| 8.2 Basic Cascade Arrangements | 126 |
| 8.3 Static Design              | 131 |
| 8.4 Multistage Circuit Design  | 131 |
| 8.5 Integrated Amplifiers      | 139 |

|                                                                                         |     |
|-----------------------------------------------------------------------------------------|-----|
| <b>9 Limiting Performance</b>                                                           |     |
| 9.1 Introduction                                                                        | 158 |
| 9.2 Input Bias Current                                                                  | 158 |
| 9.3 Gain-Bandwidth Product                                                              | 159 |
| 9.4 Noise                                                                               | 161 |
| 9.5 Stability                                                                           | 172 |
| <b>10 Evaluation</b>                                                                    |     |
| 10.1 Introduction                                                                       | 176 |
| 10.2 Signal Source                                                                      | 176 |
| 10.3 Signal Detector                                                                    | 178 |
| 10.4 Input Impedance                                                                    | 179 |
| 10.5 Output Impedance                                                                   | 180 |
| 10.6 Common Voltage Amplification                                                       | 180 |
| 10.7 Common To Differential Voltage Amplification                                       | 180 |
| 10.8 Differential Voltage Amplification                                                 | 180 |
| 10.9 Differential To Common Voltage Amplification                                       | 181 |
| 10.10 Current Amplifications                                                            | 181 |
| 10.11 Single-Ended Input Measurements                                                   | 182 |
| 10.12 Single-Ended Output Measurements                                                  | 183 |
| 10.13 Single-Ended Input And Output Measurements                                        | 184 |
| 10.14 Noise Factor Measurements                                                         | 186 |
| <b>Appendix I</b> Definitions                                                           | 191 |
| <b>Appendix II</b> Small-Signal Operation of an Unsymmetrical<br>Differential Amplifier | 199 |
| <b>Appendix III</b> Noise Factor of an Unsymmetrical Differential Amplifier             | 208 |
| <b>Selected Bibliography</b>                                                            | 216 |
| <b>Index</b>                                                                            | 223 |