

# Contents

<i>Preface</i>	<i>xxi</i>
<i>Acknowledgements</i>	<i>xxiii</i>
<b>1. Electro Magnetic Circuits</b>	<b>1</b>
Introduction	1
1.1 Magnetic Field and its Significance	2
1.2 Magnetic Circuit and its Analysis	3
1.3 Important Terms	3
1.4 Comparison between Magnetic and Electric Circuits	5
1.5 Ampere-turns Calculations	6
1.6 Series Magnetic Circuits	6
1.7 Parallel Magnetic Circuits	7
1.8 Leakage Flux	8
1.9 Magnetisation or B-H Curve	21
1.10 Magnetic Hysteresis	22
1.11 Hysteresis Loss	23
1.12 Importance of Hysteresis Loop	24
Section Practice Problems	24
1.13 Electro Magnetic Induction	28
1.14 Faraday's Laws of Electromagnetic Induction	29
1.15 Direction of Induced emf	30
1.16 Induced emf	31
1.17 Dynamically Induced emf	31
1.18 Statically Induced emf	33
1.19 Self Inductance	34
1.20 Mutual Inductance	34
1.21 Co-efficient of Coupling	35
1.22 Inductances in Series and Parallel	36
1.23 Energy Stored in a Magnetic Field	41
1.24 AC Excitation in Magnetic Circuits	42
1.25 Eddy Current Loss	44
Section Practice Problems	46

---

1.26	Electro-mechanical Energy Conversion Devices	48
1.27	Torque Development by the Alignment of Two Fields	49
1.27.1	Soft Iron Piece Placed in the Magnetic Field	49
1.27.2	Permanent Magnet Placed in the Magnetic Field	51
1.27.3	Electromagnet Placed in the Magnetic Field	53
1.28	Production of Torque	54
1.28.1	In Case of Permanent Magnet	55
1.28.2	In Case of Electromagnet	55
1.29	Production of Unidirectional Torque	57
1.29.1	By Rotating the Main Magnets	58
1.29.2	By Changing the Direction of Flow of Current in the Conductors of Electromagnet	58
1.30	emf Induced in a Rotating Coil Placed in a Magnetic Field	63
1.31	Elementary Concept of Electrical Machines	68
1.31.1	Operation of Machine as a Generator (Conversion of Mechanical Energy into Electric Energy)	68
1.31.2	Operation of Machine as a Motor	70
<i>Section Practice Problems</i>		74
<i>Review Questions</i>		74
<i>Multiple Choice Questions</i>		76
<b>2.</b>	<b>Single-Phase Transformers</b>	<b>79</b>
Introduction		80
2.1	Transformer	80
2.2	Working Principle of a Transformer	82
2.3	Construction of Transformer	82
2.3.1	Core Material	83
2.3.2	Core Construction	83
2.3.3	Transformer Winding	85
2.3.4	Insulation	88
2.3.5	Bushings	89
2.3.6	Transformer Tank	90
2.4	Simple Construction of Single-phase Small Rating (SAY 2 kVA) Transformers	91
2.5	An Ideal Transformer	94
2.6	Transformer on DC	95
2.7	emf Equation	96
<i>Section Practice Problems</i>		100
2.8	Transformer on No-load	103
2.9	Effect of Magnetisation on No-load (Exciting) Current	104
2.10	Inrush of Magnetising Current	106
<i>Section Practice Problems</i>		113
2.11	Transformer on Load	114
2.12	Phasor Diagram of a Loaded Transformer	115
2.13	Transformer with Winding Resistance	118

2.14	Mutual and Leakage Fluxes	119
2.15	Equivalent Reactance	119
<i>Section Practice Problems</i>		122
2.16	Actual Transformer	123
2.17	Simplified Equivalent Circuit	125
2.18	Short Circuited Secondary of Transformer	127
2.19	Expression for No-load Secondary Voltage	128
2.20	Voltage Regulation	129
2.21	Approximate Expression for Voltage Regulation	130
2.22	Kapp Regulation Diagram	131
<i>Section Practice Problems</i>		140
2.23	Losses in a Transformer	142
2.24	Effects of Voltage and Frequency Variations on Iron Losses	143
2.25	Efficiency of a Transformer	145
2.26	Condition for Maximum Efficiency	146
2.27	Efficiency vs Load	152
2.28	Efficiency vs Power Factor	152
2.29	All-day Efficiency	154
<i>Section Practice Problems</i>		156
2.30	Transformer Tests	158
2.31	Polarity Test	158
2.32	Voltage Ratio Test	159
2.33	Open-circuit or No-load Test	159
2.34	Separation of Hysteresis and Eddy Current Losses	161
2.35	Short Circuit Test	165
2.36	Back-to-back Test	167
<i>Section Practice Problems</i>		179
2.37	Classification of Transformers	181
2.38	Parallel Operation of Transformers	181
2.39	Necessity of Parallel Operation	182
2.40	Conditions for Parallel Operation of One-phase Transformers	182
2.41	Load Sharing between Two Transformers Connected in Parallel	184
<i>Section Practice Problems</i>		194
2.42	Auto-transformer	195
2.43	Auto-transformer vs Potential Divider	199
2.44	Saving of Copper in an Auto-transformer	199
2.45	Advantages of Auto-transformer over Two-winding Transformer	200
2.46	Disadvantages of Auto-transformers	200
2.47	Phasor Diagram of an Auto-transformer	201
2.48	Equivalent Circuit of an Auto-transformer	203
2.49	Simplified Equivalent Circuit of an Auto-transformer	203
2.50	Conversion of a Two-winding Transformer to an Auto-transformer	205
2.51	Comparison of Characteristics of Auto-transformers and Two-winding Transformers	207

---

2.52 Applications of Auto-transformers	208
<i>Section Practice Problems</i>	218
<i>Review Questions</i>	220
<i>Multiple Choice Questions</i>	221
<b>3. Three-Phase Transformers</b>	<b>224</b>
Introduction	224
3.1 Merits of Three-phase Transformer over Bank of Three Single-phase Transformers	225
3.2 Construction of Three-phase Transformers	225
3.3 Determination of Relative Primary and Secondary Windings in Case of Three-phase Transformer	227
3.4 Polarity of Transformer Windings	227
3.5 Phasor Representation of Alternating Quantities in Three-phase Transformer Connections	228
3.6 Three-phase Transformer Connections	229
3.7 Selection of Transformer Connections	233
3.7.1 Star-Star (Yy0 or Yy6) Connections	233
3.7.2 Delta-Delta (Dd0 or Dd6) Connections	236
3.7.3 Star-Delta (Yd1 or Yd11) Connections	238
3.7.4 Delta-Star (Dy1 or Dy11) Connections	239
3.7.5 Delta-Zigzag Connections	241
<i>Section Practice Problems</i>	251
3.8 Parallel Operation of Three-phase Transformers	252
3.9 Necessity of Parallel Operation of Three-phase Transformers	253
3.10 Conditions for Parallel Operation of Three-phase Transformers	254
3.11 Load Sharing between Three-phase Transformers Connected in Parallel	255
3.12 Three Winding Transformers (Tertiary Winding)	257
3.12.1 Stabilisation Provided by Tertiary Winding in Star-Star Transformer	260
3.13 Tap-changers on Transformers	265
3.14 Types of Tap-changers	266
3.14.1 No-load (or Off-load) Tap-changer	266
3.14.2 On-load Tap-changer	267
<i>Section Practice Problems</i>	268
3.15 Transformation of Three-phase Power with Two Single-phase Transformers	270
3.16 Open-Delta or V-V Connections	270
3.17 Comparison of Delta and Open Delta Connections	274
3.18 T-T Connections or Scott Connections	275
3.19 Conversion of Three-phase to Two-phase and vice-versa	277
3.20 Difference between Power and Distribution Transformers	291
3.21 Cooling of Transformers	291
3.22 Methods of Transformer Cooling	292
3.23 Power Transformer and its Auxiliaries	294

---

3.24	Maintenance Schedule of a Transformer	296
3.25	Trouble Shooting of a Transformer	297
	<i>Section Practice Problems</i>	297
	<i>Review Questions</i>	299
	<i>Multiple Choice Questions</i>	300
<b>4.</b>	<b>DC Generator</b>	<b>301</b>
	Introduction	301
4.1	DC Generator	302
4.2	Main Constructional Features	303
4.3	Simple Loop Generator and Function of Commutator	307
4.4	Connections of Armature Coils with Commutator Segments and Location of Brushes	309
4.5	Armature Winding	311
4.6	Types of Armature Winding	314
4.7	Drum Winding	315
4.8	Lap Winding	316
4.9	Numbering of Coils and Commutator Segments in Developed Winding Diagram	318
4.10	Characteristics of a Simplex Lap Winding	323
4.11	Characteristics of a Multiplex Lap Winding	327
4.12	Equalising Connections and their Necessity	327
4.13	Simplex Wave Winding	330
4.14	Dummy Coils	332
4.15	Applications of Lap and Wave Windings	338
	<i>Section Practice Problems</i>	338
4.16	emf Equation	340
4.17	Torque Equation	341
4.18	Armature Reaction	349
4.19	Calculations for Armature Ampere-turns	351
4.20	Commutation	355
4.21	Cause of Delay in the Reversal of Current in the Coil going through Commutation and its Effect	357
4.22	Magnitude of Reactance Voltage	358
4.23	Good Commutation and Poor Commutation	360
4.24	Interpoles and their Necessity	361
4.25	Compensating Winding and its Necessity	362
4.26	Methods of Improving Commutation	365
	<i>Section Practice Problems</i>	366
4.27	Types of DC Generators	368
4.28	Separately-excited DC Generators	368
4.29	Self-excited DC Generators	369
4.30	Voltage Regulation of a DC Shunt Generator	371
4.31	Characteristics of DC Generators	376

---

4.32	No-load Characteristics of DC Generators or Magnetisation Curve of DC Generator	376
4.33	Voltage Build-up in Shunt Generators	377
4.34	Critical Field Resistance of a DC Shunt Generator	378
4.35	Load Characteristics of Shunt Generator	379
4.36	Load Characteristics of Series Generators	380
4.37	Load Characteristics of Compound Generator	380
4.38	Causes of Failure to Build-up Voltage in a Generator	381
4.39	Applications of DC Generators	381
4.40	Losses in a DC Generator	382
4.41	Constant and Variable Losses	383
4.42	Stray Losses	384
4.43	Power Flow Diagram	384
4.44	Efficiency of a DC Generator	384
4.45	Condition for Maximum Efficiency	385
	<i>Section Practice Problems</i>	387
	<i>Review Questions</i>	390
	<i>Multiple Choice Questions</i>	392
<b>5.</b>	<b>DC Motors</b>	<b>395</b>
	Introduction	395
5.1	DC Motor	396
5.2	Working Principle of DC Motors	396
5.3	Back emf	397
5.4	Electro-magnetic Torque Developed in DC Motor	398
5.5	Shaft Torque	399
5.6	Comparison of Generator and Motor Action	399
5.7	Types of DC Motors	401
5.8	Characteristics of DC Motors	405
5.9	Characteristics of Shunt Motors	405
5.10	Characteristics of Series Motors	407
5.11	Characteristics of Compound Motors	408
5.12	Applications and Selection of DC Motors	409
5.12.1	Applications of DC Motors	409
5.12.2	Selection of DC Motors	410
5.13	Starting of DC Motors	411
5.14	Necessity of Starter for a DC Motor	411
5.15	Starters for DC Shunt and Compound Wound Motors	412
5.16	Three-point Shunt Motor Starter	412
5.17	Four-point Starter	414
5.18	Calculation of Step Resistances Used in Shunt Motor Starter	416
5.19	Series Motor Starter	422
	<i>Section Practice Problems</i>	423

---

5.20	Speed Control of DC Motors	428
5.21	Speed Control of Shunt Motors	428
5.21.1	Field Control Method	428
5.21.2	Armature Control Method	429
5.22	Speed Control of Separately Excited Motors	431
5.23	Speed Regulation	432
5.24	Speed Control of DC Series Motors	440
5.24.1	Armature Control Method	440
5.24.2	Field Control Method	441
5.24.3	Voltage Control Method	442
5.25	Electric Braking	451
5.26	Types of Electric Braking	453
5.26.1	Plugging	453
5.26.2	Rheostatic Braking	454
5.26.3	Regenerative Braking	455
	<i>Section Practice Problems</i>	457
5.27	Losses in a DC Machine	460
5.28	Constant and Variable Losses	461
5.29	Stray Losses	461
5.30	Power Flow Diagram	462
5.31	Efficiency of a DC Machine	462
5.32	Condition for Maximum Efficiency	463
5.33	Test Performed to Determine Efficiency of DC Machines	471
5.34	Brake Test	472
5.35	Swinburne's Test	474
5.36	Hopkinson's Test	479
5.37	Testing of DC Series Machines	487
5.38	Inspection/maintenance of DC Machines	491
5.39	Faults in DC Machines	492
5.40	Trouble Shooting in a DC Motor	492
	<i>Section Practice Problems</i>	493
	<i>Review Questions</i>	495
	<i>Multiple Choice Questions</i>	497
<b>6.</b>	<b>Synchronous Generators or Alternators</b>	<b>500</b>
	Introduction	501
6.1	General Aspects of Synchronous Machines	501
6.2	Basic Principles	502
6.3	Generator and Motor Action	503
6.4	Production of Sinusoidal Alternating emf	503
6.5	Relation between Frequency, Speed and Number of Poles	504
6.6	Advantages of Rotating Field System over Stationary Field System	504
6.7	Constructional Features of Synchronous Machines	505

6.8	Excitation Systems	509
6.8.1	DC Exciters	509
6.8.2	Static-Excitation System	510
6.8.3	Brushless Excitation System	511
<i>Section Practice Problems</i>		512
6.9	Armature Winding	513
6.10	Types of Armature Winding	513
6.11	Important Terms Used in Armature Winding	515
<i>Section Practice Problems</i>		519
6.12	Coil Span Factor	521
6.13	Distribution Factor	522
6.14	Winding Factor	524
6.15	Generation of Three-phase emf	524
6.16	emf Equation	525
6.17	Wave Shape	526
6.18	Harmonics in Voltage Wave Form	526
<i>Section Practice Problems</i>		534
6.19	Production of Revolving Field	535
6.20	Ferrari's Principle (Vector Representation of Alternating Field)	539
6.21	Production of Two-phase Rotating Magnetic Field	540
6.22	Production of Three-phase Rotating Magnetic Field	541
6.23	Rating of Alternators	542
6.24	Armature Resistance	542
6.25	Armature Leakage Reactance	543
6.26	Armature Reaction	544
6.27	Effect of Armature Reaction on emf of Alternator	546
6.28	Synchronous Reactance and Synchronous Impedance	548
6.29	Equivalent Circuit of an Alternator and Phasor Diagram	548
6.30	Expression for No-load Terminal Voltage	549
6.31	Voltage Regulation	551
6.32	Determination of Voltage Regulation	552
6.33	Synchronous Impedance Method or emf Method	552
6.33.1	Determination of Synchronous Impedance	553
6.33.2	Determination of Synchronous Reactance	555
6.34	Modern Alternators	556
6.35	Short-Circuit Ratio (SCR)	556
<i>Section Practice Problems</i>		565
6.36	Assumptions Made in Synchronous Impedance Method	566
6.37	Ampere-turn (or mmf) Method	567
6.38	Zero Power Factor or Potier Method	579
<i>Section Practice Problems</i>		591
6.39	Power Developed by Cylindrical Synchronous Generators	592

6.39.1 Power Output of an AC Generator (in Complex Form)	593
6.39.2 Real Power Output of an AC Generator	593
6.39.3 Reactive Power Output of an AC Generator	594
6.39.4 Power Input to an AC Generator (in Complex Form)	594
6.39.5 Real Power Input to an AC Generator	594
6.39.6 Reactive Power Input to an AC Generator	595
6.39.7 Condition for Maximum Power Output	595
6.39.8 Condition for Maximum Power Input	596
6.39.9 Power Equations, when Armature Resistance is Neglected	596
6.40 Two-Reactance Concept for Salient Pole Synchronous Machines	597
6.40.1 Determination of $X_d$ and $X_q$ by Low Voltage Slip Test	599
6.41 Construction of Phasor Diagram for Two-Reactance Concept	600
6.42 Power Developed by a Salient Pole Synchronous Generator	603
<i>Section Practice Problems</i>	610
6.43 Transients in Alternators	611
6.43.1 Sub-transient, Transient and Direct Reactance	613
6.44 Losses in a Synchronous Machine and Efficiency	616
6.45 Power Flow Diagram	617
6.46 Necessity of Cooling	617
6.47 Methods of Cooling	618
6.48 Preventive Maintenance	619
<i>Section Practice Problems</i>	619
<i>Review Questions</i>	620
<i>Multiple Choice Questions</i>	622
<b>7. Parallel Operation of Alternators</b>	<b>626</b>
Introduction	626
7.1 Necessity of Parallel Operation of Alternators	626
7.2 Requirements for Parallel Operation of Alternators	627
7.3 Synchronising Alternators	627
7.4 Conditions for Proper Synchronising	627
7.5 Synchronising Single-phase Alternators	629
7.5.1 Dark Lamp Method	629
7.5.2 Bright Lamp Method	631
7.6 Synchronising Three-phase Alternators	631
7.6.1 Three Dark Lamps Method	632
7.6.2 Two Bright and One Dark Lamp Method	633
7.7 Synchronising Three-phase Alternators using Synchroscope	635
7.8 Shifting of Load	636
7.9 Load Sharing between Two Alternators	637
<i>Section Practice Problems</i>	646
7.10 Two Alternators Operating in Parallel	647
7.11 Synchronising Current, Power and Torque	647

---

9.40	Results Obtainable from Circle Diagram	785
9.41	Maximum Quantities	785
9.42	Significance of Some Lines in the Circle Diagram	786
<i>Section Practice Problems</i>		793
9.43	Effect of Space Harmonies	795
9.43.1	Cogging in Three-phase Induction Motors	795
9.43.2	Crawling in Three-phase Induction Motors	795
9.44	Performance Curves of Induction Motors	796
9.45	Factors Governing Performance of Induction Motors	798
9.46	High Starting Torque Cage Motors	798
9.46.1	Deep Bar Cage Rotor Motors	799
9.46.2	Double Cage Induction Motor	800
9.47	Motor Enclosures	807
9.48	Standard Types of Squirrel Cage Motor	810
9.48.1	Class A Motors	811
9.48.2	Class B Motors	811
9.48.3	Class C Motors	811
9.48.4	Class D Motors	812
9.48.5	Class E Motors	812
9.48.6	Class F Motors	813
9.49	Advantages and Disadvantages of Induction Motors	813
9.49.1	Squirrel Cage Induction Motors	813
9.49.2	Slip-ring Induction Motors	814
9.50	Applications of Three-phase Induction Motors	814
9.51	Comparison of Squirrel Cage and Phase Wound Induction Motors	815
9.52	Comparison between Induction Motor and Synchronous Motor	815
9.53	Installation of Induction Motors	816
9.54	Preventive Maintenance of Three-phase Induction Motors	818
<i>Section Practice Problems</i>		819
<i>Review Questions</i>		820
<i>Multiple Choice Questions</i>		822
<b>10.</b>	<b>Starting Methods and Speed Control of Three-phase Induction Motors</b>	<b>828</b>
Introduction		828
10.1	Necessity of a Starter	829
10.2	Starting Methods of Squirrel Cage Induction Motors	829
10.2.1	Direct on Line (D.O.L.) Starter	829
10.2.2	Stator Resistance (or Reactance) Starter	831
10.2.3	Star-Delta Starter	832
10.2.4	Auto-transformer Starter	834
10.3	Rotor Resistance Starter for Slip Ring Induction Motors	836
<i>Section Practice Problems</i>		844
10.4	Speed Control of Induction Motors	844

10.5	Speed Control by Changing the Slip	845
10.5.1	Speed Control by Changing the Rotor Circuit Resistance	845
10.5.2	Speed Control by Controlling the Supply Voltage	846
10.5.3	Speed Control by Injecting Voltage in the Rotor Circuit	847
10.6	Speed Control by Changing the Supply Frequency	847
10.7	Speed Control by Changing the Poles	847
10.8	Speed Control by Cascade Method	848
10.9	Speed Control by Injecting an emf in the Rotor Circuit	850
10.9.1	Kramer System of Speed Control	851
10.9.2	Scherbius System of Speed Control	851
<i>Section Practice Problems</i>		854
<i>Review Questions</i>		854
<i>Multiple Choice Questions</i>		855
<b>11.</b>	<b>Single-Phase Motors</b>	<b>857</b>
Introduction		857
11.1	Classification of Single-phase Motors	857
11.2	Single-phase Induction Motors	858
11.3	Nature of Field Produced in Single Phase Induction Motors	859
11.4	Torque Produced by Single-phase Induction Motor	860
11.5	Equivalent Circuit of Single-phase Induction Motor	861
11.6	Rotating Magnetic Field from Two-phase Supply	866
11.7	Methods to make Single-phase Induction Motor Self-starting	870
11.8	Split Phase Motors	871
11.9	Capacitor Motors	875
<i>Section Practice Problems</i>		878
11.10	Shaded Pole Motor	879
11.11	Reluctance Start Motor	880
11.12	Single-phase Synchronous Motors	881
11.13	Reluctance Motors	882
11.14	Hysteresis Motors	884
11.15	AC Series Motor or Commutator Motor	885
11.16	Universal Motor	886
11.17	Comparison of Single-phase Motors	888
11.18	Trouble Shooting in Motors	889
<i>Section Practice Problems</i>		890
<i>Review Questions</i>		891
<i>Multiple Choice Questions</i>		892
<b>12.</b>	<b>Special Purpose Machines</b>	<b>893</b>
Introduction		893
12.1	Feedback Control System	893
12.2	Servomechanism	894

---

12.3	Servomotors	894
12.4	DC Servomotors	895
12.4.1	Field-controlled DC Servomotors	895
12.4.2	Armature-controlled DC Servomotors	895
12.4.3	Series Split-field DC Servomotors	896
12.4.4	Permanent-magnet Armature-controlled DC Servomotor	896
12.5	AC Servomotors	897
12.6	Schrage motor	898
<i>Section Practice Problems</i>		903
12.7	Brushless Synchronous Generator	903
12.7.1	Brushless DC Generator	905
12.8	Brushless Synchronous Motor	905
12.9	Three-brush (or Third-brush) Generator	906
12.10	Brushless DC Motors	907
12.11	Stepper Motors	908
12.11.1	Permanent-magnet (PM) Stepper Motor	909
12.11.2	Variable-reluctance (VR) Stepper Motor	912
<i>Section Practice Problems</i>		913
12.12	Switched Reluctance Motor (SRM)	914
12.13	Linear Induction Motor (LIM)	915
12.14	Permanent Magnet DC Motors	917
12.15	Induction Generator	920
12.16	Submersible Pumps and Motors	922
12.17	Energy Efficient Motors	926
<i>Section Practice Problems</i>		929
<i>Review Questions</i>		929
<i>Multiple Choice Questions</i>		930
<i>Open Book Questions</i>		933
<i>Index</i>		949